# week4\_solution

## Aman Kumar EE21B013 <ee21b013@smail.iitm.ac.in>

March 1, 2023

#### 1 About Code and How to run:

- This is a simple .ipynb file just run it in jupyter notebook -I have divided the program in different function so the previous block of code is might be required for getting the correct output form the current block.
- So to avoid some unusual output run the code serially.
- The function are well defind and **comments** have been given where ever required.
- As the code is itself too long and i think it is self explanatory because i tried to use as much similar name of variable to what they are getting used for inside the code ,so why i have not given very large explanation on working of function
- One can easily understand the codes if he/she goes **serially and manually**.
- I have stored output of Both the **topological\_sort and EVENT\_DRIVEN** seperately in two output files named :
- for EVENT DRIVEN=> file name is -EVENT DRIVEN OUTPUT.txt
- for TOPOLOGICAL SORT=> file name is topological Sort.txt
- $\bullet~$  If you have any difficulty in reading or understanding function anywhere just ask me to explain

[329]: def pri(A):
 for i in A:
 print(i)

## 1.1 Below Functions are defined for performing logical operation to get output

```
[330]: #Functions defined for performing logical operation

def andFunc(a,b):
    if(a==0 or b==0):
        return 0

    else:
        return 1

def orFunc(a,b):
    if(a==1 or b==1):
        return 1

    else:
        return 0

def invFunc(a):
```

```
if(a==1):
         return 0
    else:
         return 1
def norFunc(a,b):
    if(a==1 or b==1):
         return 0
    else:
         return 1
def nandFunc(a,b):
    if(a==0 or b==0):
         return 1
    else:
         return 0
def xorFunc(a,b):
    if ((a==1 \text{ and } b==0) \text{ or } (a==0 \text{ and } b==1)):
         return 1
    else:
         return 0
def xnorFunc(a,b):
    if ((a==1 \text{ and } b==0) \text{ or } (a==0 \text{ and } b==1)):
         return 0
    else:
         return 1
```

### 1.2 The below code is for Reading the input file

ckt\_detail=[]

for line in ckt\_netlist:

```
[331]: # Function for Reading of gate and circuit information

def read_netlist(filename):
    with open(filename,'r') as mainfile:
        file_storage=mainfile.readlines()
        return file_storage

[332]: # Fucntion for reading of inputs

def read_input(filename):
    with open(filename,'r') as mainfile:
        file_storage=mainfile.readlines()
        return file_storage

[333]: ckt_netlist=read_netlist('/Users/amankumar/Documents/semester4/Applied_
Programming Lab(APL)/Assignment4/benchmarks/c17.net')
```

```
ckt_detail.append(line)
ckt_input=read_input('/Users/amankumar/Documents/semester4/Applied ProgrammingL
 inputckt_detail=[]
for line in ckt input:
    inputckt_detail.append(line.rstrip('\n').split())
print('primary input at different time instant : ')
pri(inputckt_detail)
primary_input at different time instant :
['N1', 'N2', 'N3', 'N6', 'N7']
['0', '1', '0', '0', '0']
['0', '0', '1', '0', '0']
['1', '0', '0', '0', '0']
['0', '0', '1', '1', '1']
['1', '1', '1', '1', '1']
['1', '1', '1', '0', '0']
['1', '1', '1', '1', '0']
['1', '1', '0', '0', '0']
['0', '1', '1', '0', '1']
['0', '0', '1', '1', '0']
```

### 1.3 SECTION: Making of graph using inbuilt Function by adding edges

```
[334]: import networkx as nx
      g=nx.DiGraph()
      connection={} # For storing connection like storing of connections based on
        →output (i.e. key is output and the value is connected elements)
      for i in range(len(ckt_detail)):
           if(ckt_detail[i].split()[1]=='inv' or ckt_detail[i].split()[1]=='buf'):
               connection[ckt_detail[i].split()[3]]=ckt_detail[i].split()[1:
        →len(ckt_detail[i])-2]
               connection[ckt_detail[i].split()[4]]=ckt_detail[i].split()[1:
        →len(ckt_detail[i])-2]
      print(connection)
      for ele in connection:
           if(connection[ele][0] == 'inv' or connection[ele][0] == 'buf'):
               g.add_edges_from([(connection[ele][1],connection[ele][2])])
               # nx.set_node_attributes(g,{connection[ele][2]:ele})
          else:
        -add_edges_from([(connection[ele][1],connection[ele][3]),(connection[ele][2],connection[ele]
               # nx.set_node_attributes(q, {connection[ele][3]:ele})
```

```
print(g)
{'N22': ['nand2', 'n_3', 'n_0', 'N22'], 'N23': ['nand2', 'n_3', 'n_2', 'N23'],
'n_3': ['nand2', 'n_1', 'N2', 'n_3'], 'n_2': ['nand2', 'n_1', 'N7', 'n_2'],
'n_0': ['nand2', 'N1', 'N3', 'n_0'], 'n_1': ['nand2', 'N3', 'N6', 'n_1']}
DiGraph with 11 nodes and 12 edges
```

## Topological sort for ordering of output and input of gate

### 2.0.1 Error handling

```
[335]: error=False
      try:
           nl = list(nx.topological sort(g))
           print('Nodes in topological order', nl)
       except:
           error=True
           print("!!! ERRROR : CYCLIC GRAPH")
      Nodes in topological order ['N2', 'N7', 'N1', 'N3', 'N6', 'n_0', 'n_1', 'n_3',
      'n_2', 'N22', 'N23']
[358]: primary_input={}
       print(inputckt_detail[0])
       for i in range(len(inputckt_detail[0])):
           primary_input.update({inputckt_detail[0][i]:[]})
       for i in range(1,len(inputckt_detail)):
           for j in range(len(inputckt_detail[0])):
               primary_input[inputckt_detail[0][j]].append(int(inputckt_detail[i][j]))
       try:
           for ele in primary_input:
               for value in primary input[ele] :
                   if value==0 or value ==1:
                       continue
                   else:
                       raise ValueError
       except ValueError:
           print('!!! ERROR WRONG INPUT FORMAT')
       print('Primary Inputs are : ')
       print(primary_input)
       print()
       print('connetion are means in dictionary connection output is key and other ⊔
        →things related to output are its value : ')
       print(connection)
      ['N1', 'N2', 'N3', 'N6', 'N7']
```

Primary Inputs are :

```
{'N1': [0, 0, 1, 0, 1, 1, 1, 1, 0, 0], 'N2': [1, 0, 0, 0, 1, 1, 1, 1, 1, 1, 0],
'N3': [0, 1, 0, 1, 1, 1, 1, 0, 1, 1], 'N6': [0, 0, 0, 1, 1, 0, 1, 0, 0, 1],
'N7': [0, 0, 0, 1, 1, 0, 0, 0, 1, 0]}

connetion are means in dictionary connection output is key and other things
related to output are its value :
{'N22': ['nand2', 'n_3', 'n_0', 'N22'], 'N23': ['nand2', 'n_3', 'n_2', 'N23'],
'n_3': ['nand2', 'n_1', 'N2', 'n_3'], 'n_2': ['nand2', 'n_1', 'N7', 'n_2'],
'n_0': ['nand2', 'N1', 'N3', 'n_0'], 'n_1': ['nand2', 'N3', 'N6', 'n_1']}
```

### 3 EXPLANATION OF BELOW CODE

- FUNCTION topo\_sort\_fun: takes 3 input (connection ,input\_detail,primary\_input)
- Based on above topological sorting I am just traversing the topological order and calculaing the value of output accordingly.
- after calculating all the output of all the nodes i am storing the output in final output
- after that there is a file writing process that will write the output correspondingly in a file named topological\_Sort.txt.

```
[347]: import copy
       # Function topo sort find the solution based on topological sorting ordering
       def topo sort func(connection,inputc8 detail,primary input):
               print('!!! ERRROR CYCLIC GRAPH ')
               return
           final_output=[]
           for i in range(1,len(inputc8_detail)):
               output_detail={} #storing dictionary for output
               for ele in nl:
                   if(ele in primary_input.keys()):
                       output_detail.update({ele:primary_input[ele][i-1]})
                   else:
                       if(connection[ele][0] == 'and2'):
                           output_detail.update({ele:
        andFunc(output_detail[connection[ele][1]],output_detail[connection[ele][2]])})
                       if(connection[ele][0] == 'or2'):
                           output detail.update({ele:
        GorFunc(output_detail[connection[ele][1]],output_detail[connection[ele][2]])})
                       if(connection[ele][0] == 'inv'):
                           output_detail.update({ele:
        →invFunc(output_detail[connection[ele][1]])})
                       if(connection[ele][0] == 'nand2'):
                           output detail.update({ele:
        anandFunc(output_detail[connection[ele][1]],output_detail[connection[ele][2]])})
                       if(connection[ele][0] == 'nor2'):
                           output_detail.update({ele:
        onorFunc(output_detail[connection[ele][1]],output_detail[connection[ele][2]])})
```

```
if(connection[ele][0] == 'xor2'):
                    output_detail.update({ele:
 axorFunc(output_detail[connection[ele][1]],output_detail[connection[ele][2]])})
                if(connection[ele][0] == 'xnor2'):
                    output_detail.update({ele:
 wxnorFunc(output_detail[connection[ele][1]],output_detail[connection[ele][2]])})
                if(connection[ele][0] == 'buf'):
                    output_detail.update({ele:
 →output_detail[connection[ele][1]]})
        # print(f"for input \{i\} values of all noes are :") # Uncomment this and
 the below line to view the output at differnt input in file
        # print(output_detail)
        final_output.append(copy.deepcopy(output_detail))
    return final output
topo_sort_Output=topo_sort_func(connection,inputckt_detail,primary_input)
# print('topo sort Output : ')
# print(topo_sort_Output)
# File writing for the solution
with open('topological Sort.txt','w') as f:
    for nodes in sorted(n1):
        f.write(f'{nodes:<10}')
    f.write("\n")
    for element in topo_sort_Output:
        for ele in sorted(element.keys()):
            f.write(f'{element[ele]:<10}')</pre>
        f.write('\n')
```

### 4 EVENT DRIVEN SOLUTION

```
[342]: # connections
# print(connection) #storage dictionary according to output key is output and
other things are stored in lsit
# print(inputc8_detail) # storage after reading of input file
# print(primary_input) # store primary input values
```

# 5 Explantaiton of below function

- Function is taking three argument-> connection (stores information about circuit), in-put\_detail(details of input),primaryinput(stores primary input and its values at different time instant) all these three are defined above and it is passed in the parameter just after the function end when calling the function.
- Inside the function I am using the queue to sotre and do the operation needed for evnet driven

approach.

- Inside the function iterating over the different instant of input and checking the input when the input changes i am just appending that element in the queue and then iterating over the queue till the queue is not empty and assigning the updated output of different nodes.
- I have used input\_connection to store the output that will be affected by changing the that particular input.
- final\_output is storing the final output .

•

```
[343]: import copy
       # print(primary input)
       def Event_Driven_solution(connection,input_detail,primary_input):
               print('!!! ERRROR CYCLIC GRAPH ')
               return
           final_output=[]
           final_output.clear()
           updated output={} # dictionary for storing the output at different ⊔
        ⇔changing output
           updated_output.clear()
           queue=[]
           # print(connection)
           # storing the connection like which are the outut corresponding to a_{\sqcup}
        →particular input inside the input_connection
           intput connnection={}
           for ele in connection:
               if(connection[ele][0]!='inv' and connection[ele][0]!='buf'):
                   intput_connnection.update({connection[ele][1]:[]})
                   intput_connnection.update({connection[ele][2]:[]})
               else:
                   intput_connnection.update({connection[ele][1]:[]})
           # Populating the input_connection dictonary
           for ele in connection:
               # print(ele)
               if(connection[ele][0]!='inv' and connection[ele][0]!='buf'):
                   current_ele1=intput_connnection[connection[ele][1]]
                   current_ele1=current_ele1+[ele]
                   current_ele2=intput_connnection[connection[ele][2]]
                   current_ele2=current_ele2+[ele]
                   intput_connnection.update({connection[ele][1]:current_ele1})
                   intput_connnection.update({connection[ele][2]:current_ele2})
```

```
else:
           current_ele1=intput_connnection[connection[ele][1]]
           current_ele1=current_ele1+[ele]
           intput_connnection.update({connection[ele][1]:current_ele1})
   # print('input connection : ') #Uncomment this and below three lines it_{\square}
⇒will show the input connection means storing what are
   # print(intput_connnection) #different output connected to a given input
   # print(primary_input)
  queue.clear()
   # print(len(input_detail))
  for i in range(len(input_detail)-1):
      for ele in primary_input:
           if(i==0):
               queue.append(ele)
               updated_output.update({ele:primary_input[ele][i]})
           else:
               if(primary_input[ele][i]!=primary_input[ele][i-1]):
                   queue.append(ele)
                   updated_output.update({ele:primary_input[ele][i]})
               else:
                   updated_output.update({ele:primary_input[ele][i]})
       # Do the operation while queue is not empty
       while(len(queue)>0):
           curr_vertex=queue.pop(0)
           if curr_vertex in primary_input.keys():
               if curr_vertex in intput_connnection.keys():
                   for all_output in intput_connnection[curr_vertex]:
                       queue.append(all_output)
           else:
               if connection[curr_vertex][0]!='inv' and__
⇔connection[curr_vertex][0]!='buf':
                   inp1=connection[curr_vertex][1]
                   inp2=connection[curr_vertex][2]
                   if inp1 in updated_output.keys() and inp2 in updated_output.
→keys():
                       if connection[curr_vertex][0] == 'and2':
                           updated output.update({curr vertex:
-andFunc(updated_output[inp1],updated_output[inp2])})
                       elif connection[curr_vertex][0] == 'or2':
                           updated_output.update({curr_vertex:
⇔orFunc(updated_output[inp1],updated_output[inp2])})
                       elif connection[curr_vertex][0] == 'nand2':
                           updated_output.update({curr_vertex:
→nandFunc(updated_output[inp1],updated_output[inp2])})
```

```
elif connection[curr_vertex][0] == 'nor2':
                            updated_output.update({curr_vertex:
 anorFunc(updated_output[inp1], updated_output[inp2])})
                        elif connection[curr vertex][0] == 'xor2':
                            updated_output.update({curr_vertex:
 axorFunc(updated output[inp1], updated output[inp2])})
                        elif connection[curr_vertex][0] == 'xnor2':
                            updated_output.update({curr_vertex:

¬xnorFunc(updated_output[inp1], updated_output[inp2])})

                    else:
                        queue.append(curr_vertex)
                        continue
                    if curr_vertex in intput_connnection.keys():
                        for all_output in intput_connnection[curr_vertex]:
                            queue.append(all_output)
                else:
                    inp1=connection[curr_vertex][1]
                    if(inp1 in updated_output.keys()):
                        if connection[curr_vertex][0] == 'inv':
                            updated_output.update({curr_vertex:
 →invFunc(updated_output[inp1])})
                        elif connection[curr vertex][0] == 'buf':
                            updated_output.update({curr_vertex:
 →updated_output[inp1]})
                    else:
                        queue.append(curr_vertex)
                        continue
                    if curr_vertex in intput_connnection.keys():
                        for all_output in intput_connnection[curr_vertex]:
                            queue.append(all_output)
        # print(f'Different Nodes value for input at {i} are : ')# Uncomment_
 these two lines for showing output at different instance of time
        # print(updated_output)
        final_output.append(copy.deepcopy(updated_output))
    return final_output
event driven Output=Event Driven solution(connection,inputckt detail,primary input)
 → #Calling of Event_Driven function for getting output
# Writing the Output in file EVENT_DRIVEN_OUTPUT.txt
with open('EVENT_DRIVEN_OUTPUT.txt','w') as f:
    for nodes in sorted(nl):
        f.write(f'{nodes:<10}')
    f.write("\n")
    for element in event_driven_Output:
        for ele in sorted(element.keys()):
```

```
f.write(f'{element[ele]:<10}')
f.write('\n')</pre>
```

```
[345]: print('The time taken by Event_driven_solution : ')
%timeit Event_Driven_solution(connection,inputckt_detail,primary_input)
print('the time taken by topo_sort_function : ')
%timeit topo_sort_func(connection,inputc8_detail,primary_input)
```

```
The time taken by Event_driven_solution : 146 \mu s \pm 300 ns per loop (mean \pm std. dev. of 7 runs, 10,000 loops each) the time taken by topo_sort_function : 94.2 \mu s \pm 618 ns per loop (mean \pm std. dev. of 7 runs, 10,000 loops each)
```

In some cases the time taken by topological sort may be less than the time taken by Event\_driven approach But in large no of cases we will observe that the time taken by event driven approach is less because if the input changes in small no than the event driven approach is a way bettr than the topological sort because we need to update only the corresponding output but in topological sort we need to iterate the whole vertex each time to update the output at each terminal respectively.